

1. Let R_3 is changed to $R_3 + \Delta R_3$, $R_1 = R_2 = R_3 = R_4 = 120\Omega$

$$V_o = V_s \frac{R_2 R_3}{(R_2 + R_3)^2} \left(\frac{\Delta R_3}{R_3} \right), \text{ Gauge factor} = 2.1$$

$$20 \times 10^{-3} = \frac{10 \times (120)^2}{4 \times 120^2} \left(\frac{\Delta R_3}{R_3} \right)$$

$$\frac{\Delta R_3}{R_3} = 8 \times 10^{-3}, \text{ Gauge factor} = \frac{\left(\frac{\Delta R_3}{R_3} \right)}{\epsilon_t}$$

$$\text{Strain} = \frac{8 \times 10^{-3}}{2.1} = \underline{\underline{3.8 \times 10^{-3}}}$$

Sol
2

Bridge supply voltage $V_s = E$

$E = ?$

Strain Gauge Resistance = 1000Ω

Gauge factor = 2.1

(a) - In balance condⁿ total current supplied by supply

$$= 20 \text{ mA} \times 2 = 40 \text{ mA}$$

$$\text{Equivalent resistance offered to supply} = (1000 + 1000) \parallel (1000 + 1000) \\ = 1000\Omega$$

$$E = 40 \times 10^{-3} \times 1000$$

$$= 40 \text{ Volt}$$

(b) In the arrangement R_1 & R_3 measures axial strain and R_2 & R_4 measures the circumferential strain

$$\text{Axial strain in cylinder} = \frac{\text{Force}}{\text{Young modulus} \times \text{area}}$$

$$= \frac{10^5}{2.07 \times 10^8 \times 2 \times 10^{-4}}$$

$$= 2.415 \times 10^{-3}$$

$$\frac{\Delta R}{R} = \text{Strain} \times \text{Gauge factor} = 2.415 \times 10^{-3} \times 2.1$$

Thettag Thevenin voltage across current detector $= (V_0)_{Th}$


$$(V_0)_{Th} = \frac{V_s (R_2 R_3)}{(R_2 + R_3)^2} \frac{\Delta R}{R}$$

$$(V_0)_{Th} = \frac{40 \times R^2}{4 R^2} \frac{\Delta R}{R} = \frac{40 \times 2.415 \times 10^{-3} \times 2.1}{4}$$

$$(V_0)_{Th} = 5.145 \times 10^{-2} \text{ volt}$$

$$(R_{Th}) = (1000 + 1000) \parallel (1000 + 1000) = 1000 \Omega$$
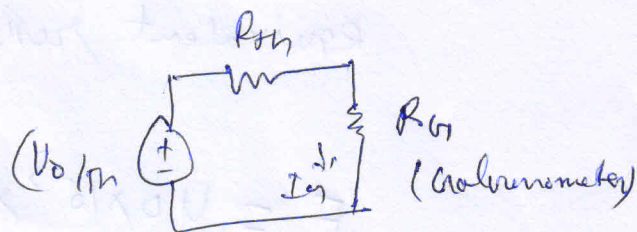
$$I_n = \frac{(V_0)_{Th}}{(R_{Th} + R_n)} = \frac{5.145 \times 10^{-2}}{1000 + 500}$$



$$= 3.4 \times 10^{-5} \text{ A}$$

With signal enhancement factor $I_n = 2.6 \times 3.4 \times 10^{-5}$
 $= 8.8 \times 10^{-5} \text{ A}$

Solⁿ 3 $V_{Th} = V_{ad} - V_{ac} = 5V \times \left(\frac{100}{100+200} - \frac{1000}{1000+1005} \right)$ (3)

$$= 2.77 \text{ mV}$$

$$R_{Th} = (100 \parallel 200) + (1000 + 1005) = 734 \Omega$$

$$I_g = \frac{V_{Th}}{R_{Th} + R_g} = \frac{2.77 \text{ mV}}{734 + 100} = \underline{3.32 \mu A}$$

Galvanometer deflection $\Rightarrow d = 3.32 \mu A \times \frac{10 \text{ mm}}{\mu A}$

$$\boxed{d = 33.2 \text{ mm}}$$

Solⁿ 4: at Balance Condⁿ

Real part $32.7 \times 100 = (1.36 + R_4) 100 \Rightarrow R_4 = \underline{31.34 \Omega}$

Imaginary $L_1 \times 100 = L_4 \times 100 \Rightarrow L_1 = L_4 = \underline{47.8 \text{ mH}}$

Solⁿ 5:

$$R_3 = 240 \Omega$$

$$L_3 = C R_2 R_4 = \underline{0.12 \text{ H}}$$

Solⁿ 6:

$f = 50 \text{ Hz}, \quad \omega = 314.2 \text{ rad/sec}$

$$R_1 = \frac{\omega^2 \times (0.38 \times 10^{-6})^2 + 833 \times 16800 \times 1000}{1 + \omega^2 833^2 (0.38 \times 10^{-6})^2}$$
$$= \underline{\underline{210 \Omega}}$$

$$L_1 = \frac{\omega^2 \times 1000 \times 3.8 \times 10^{-6}}{1 + \omega^2 833^2 \times (0.38 \times 10^{-6})^2} = \underline{\underline{6.38 \text{ H}}}$$

Solⁿ 7:

$$r_1 = 3.65 \Omega, \quad C_1 = 0.7112 \mu\text{F}$$

dissipating factor $D_1 = \omega C_1 R_1 = \underline{\underline{0.007}}$

Solⁿ 8:

$$C = 259.3 \text{ pF}$$

$$R = 0.429 \text{ M}\Omega, \quad \text{P.f.} = \omega R C_2 = \underline{\underline{0.035}}$$

Solⁿ 9:

$$(a) \quad R = \underline{\underline{100 \Omega}}$$

$$(b) \quad f = \underline{\underline{796 \text{ Hz}}}$$